

**EUROPEAN ORGANIZATION FOR NUCLEAR RESEARCH  
ORGANISATION EUROPEENNE POUR LA RECHERCHE NUCLEAIRE**

**CERN - PS DIVISION**

**PS/ RF/ Note95-08**

**2W - 0.3 - 20 MHZ AMPLIFIER  
(PS/RF-HC 3193)**

**M. Paoluzzi**

**Geneva, Switzerland  
15 March 1995**

## 1. CIRCUIT DESCRIPTION

The amplifier (Figure 1) is composed of a single stage using a Motorola rf power mosfet type MRF136 and working in class A.

A 2 ways power combiner (T1, T2, R1, R2) allows two independent signals to be applied to the mosfet gate and ensures adequate (>26 dB) insulation between the two input ports.

Q1 amplifies the gate signal which is then applied to the output port whose matching to  $50 \Omega$  is ensured by R7, R8.

The amplifier transfer function, input ports insulation and group delay are plotted in Figures 2, 3 and 4 respectively.

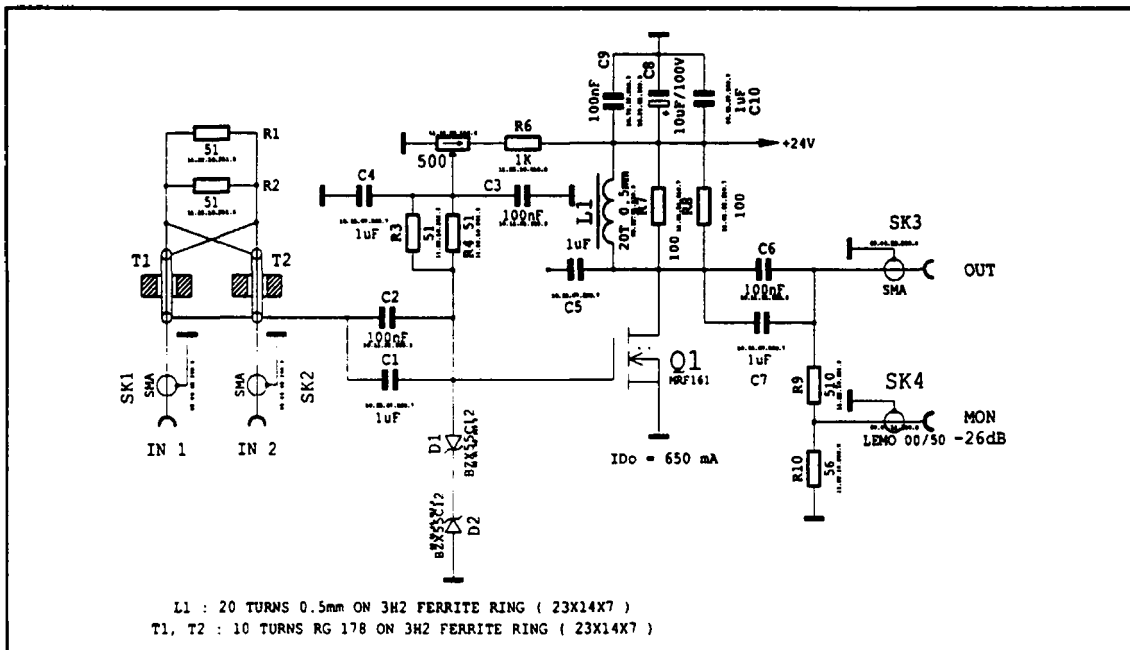


Figure 1. Amplifier Circuit Diagram.

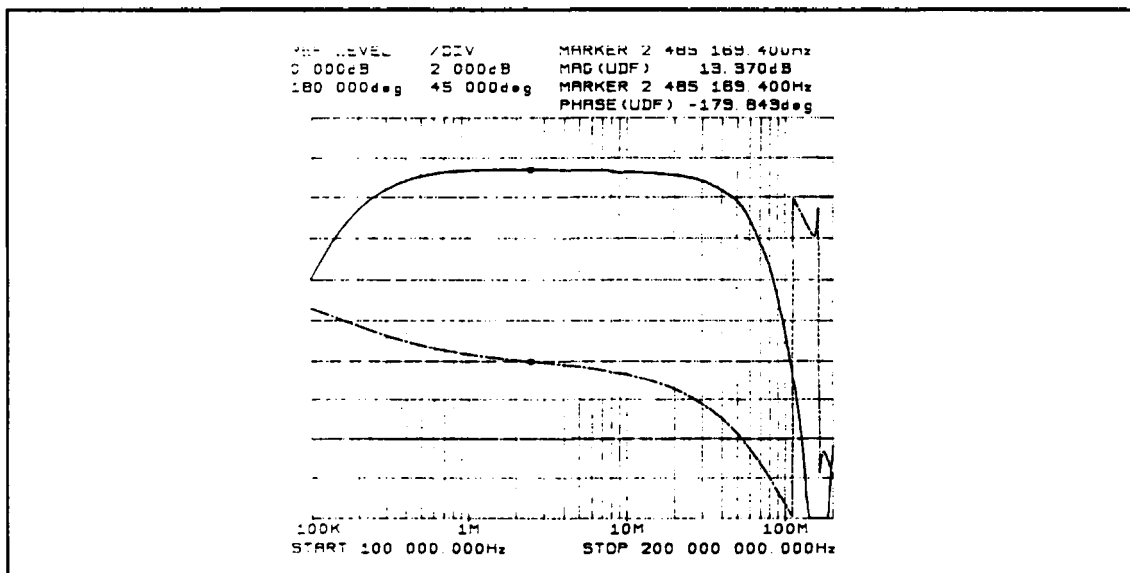


Figure 2. Amplifier Transfer Function.

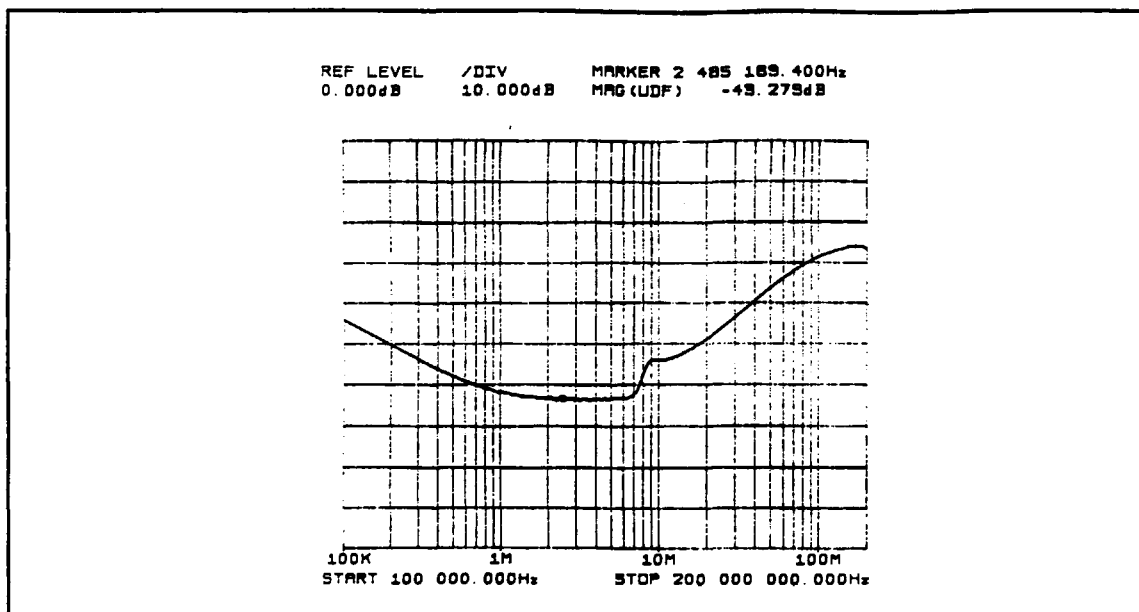


Figure 3. Amplifier Input Ports Insulation.

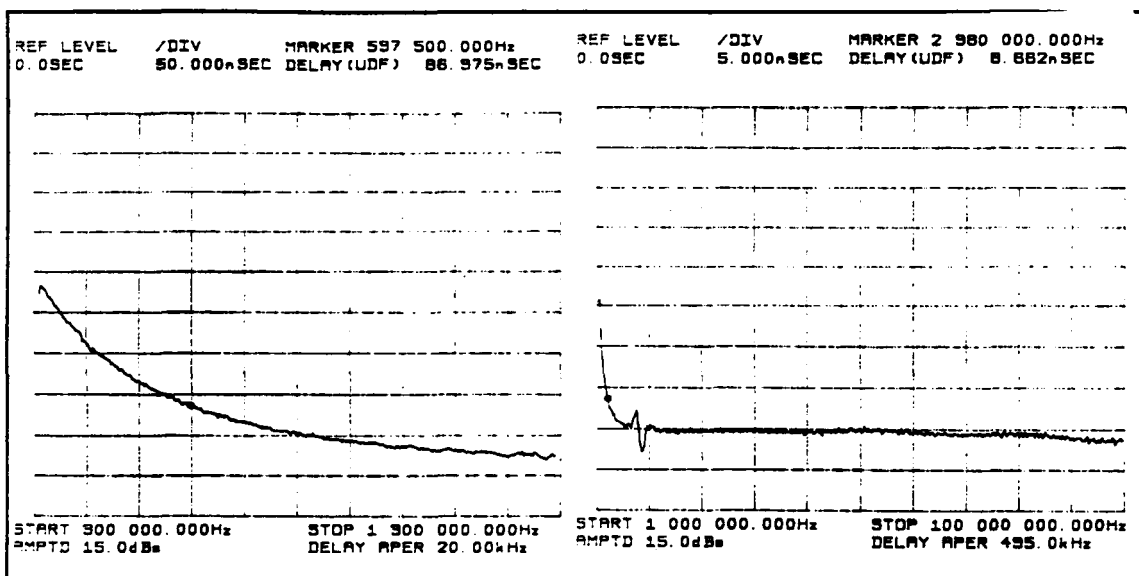


Figure 4. Amplifier Group Delay.

## 2. ADJUSTMENT

<b>1</b>	<b>Preliminary Adjustment</b>
<b>1.1</b>	By visual inspection verify that the module does not present evident manufacture errors and verify that it has been properly cleaned.
<b>1.2</b>	Preset P1 at minimum.
<b>1.3</b>	Supply the circuit with 24 V and adjust P1 so as to obtain a rest-current of 650 mA.

<b>2</b>	<b>RF Measurements</b>
<b>2.1</b>	Using the test set-up shown in Figure 5 measure the amplifier transfer function ( B/R ) and input ports insulation ( A/R). Verify that the Gain at 2.5 MHz is 13.5 dB +/- 0.5 dB. Verify that the -1 dB bandwidth is at least 0.3 MHz to 40 MHz. Verify the in the band 0.3 MHz - 20 MHz the insulation is better than 26 dB
<b>3</b>	<b>Labeling</b>
<b>3.1</b>	Put a drop of paint on P1.
<b>3.2</b>	Label the module 'OK+Date'

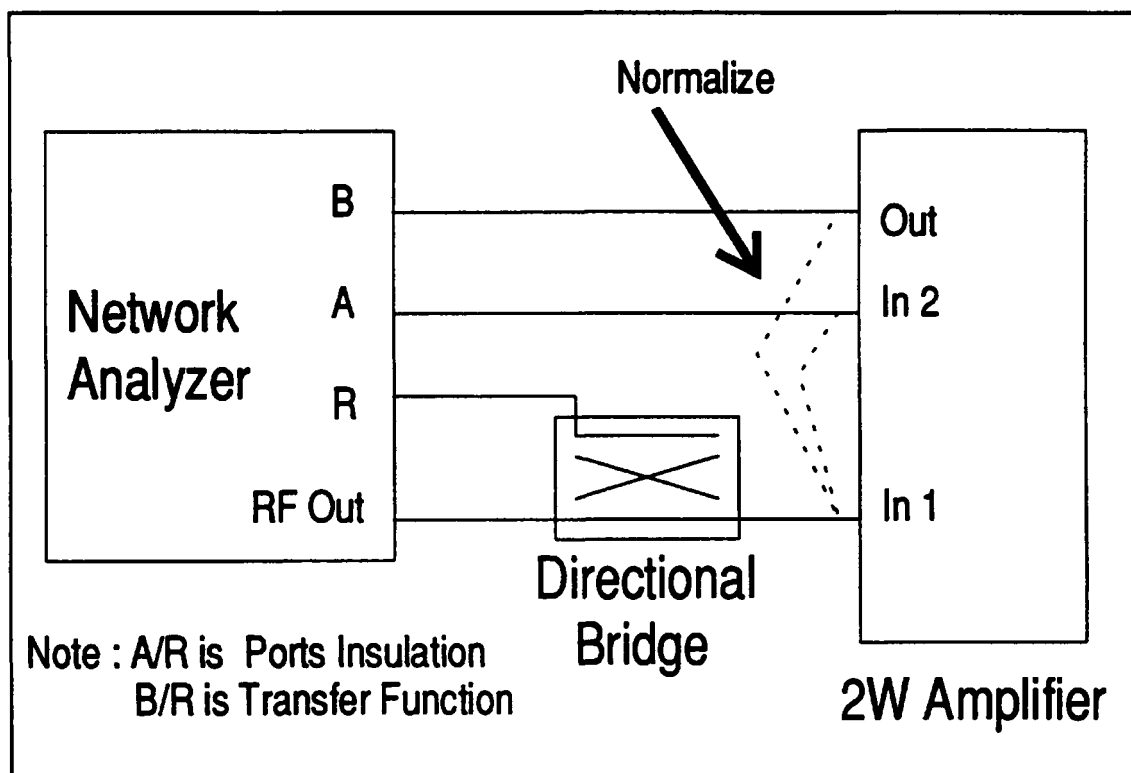


Figure 5. RF Measurement Set-Up.

Distribution :

R. Garoby  
PS-RF-HC Section