
Cell Balancing Design Guidelines

*Author: Rich DelRossi
Microchip Technology Inc.*

CELL BALANCE APPLICATIONS

When battery packs are built with multiple cells in series, cell balancing becomes an issue. Cell balance occurs when all the individual cells in series have the same capacity, and as a result, the same voltage. This is not a concern for cells in parallel since parallel cells will balance each other with mutually applied voltage.

For cells in series, this is a concern because it is the weakest cell that determines the empty point for the battery. The lowest capacity cell will have the lowest voltage and cause end of discharge conditions in battery gauges and under voltage conditions in safety circuits to trip. Thus an undercharged series cell will cause the entire pack to have less lifetime. During charge, the highest voltage cell will trip the battery gauge or safety circuit, and not allow the lower charged cells to fully charge. For this reason, cell balancing circuitry should be considered for optimum runtime for any cell chemistry that has difficulty maintaining a balance.

Cell imbalance occurs when cells do not hold the same amount of charge. It is important in the manufacturing process to match the capacitance of the cells to achieve cell balance. Since the capacitance of the cell is the coulombs per volt, then cells of the same voltage will contain the same charge. This is done well today for Lithium Ion cells, but for Lithium Polymer cells, it is difficult to match the capacitance. Thus same voltage cells could vary somewhat in charge. It is important then for Lithium Polymer cells to utilize cell balancing to ensure the longest possible run time.

CELL BALANCING IMPLEMENTATIONS

In order to keep cells balanced, the individual voltages must be monitored. When a voltage difference between cells becomes too large, a circuit can be enabled to draw more current from the higher cells. Power transistors connected to each cell can be turned on to bleed high cells when necessary. During a discharge, the transistor path will draw more current from high cells. During charge, the transistor path will take some charge current away from high cells. More balance current will occur near end of discharge and end of charge than in the middle of the cycles due to the flatness of the voltage curve in the middle. Also it may not be desirable to drain balance current near end of discharge, thus a controlling circuit can be used to only drain balance current near end of charge on a charging cycle. The PS401 can provide this monitoring and control.

A power transistor is necessary due to the amount of current that needs to be drained. For example, if there is an imbalance of 100 mV between cells, this may correspond to 200 mAH of charge (this will vary between cell manufacturers and operating conditions). It would take 2 hours to balance these cells with a balancing current of 100 mA. This is too much current to drain internally in an integrated circuit, thus it requires power transistors controlled by the IC. There are cell balancing safety IC's available that can sink up to 10 mA of balancing current, but this would take the above example 20 hours to balance. A trade off must be made between time to balance and power dissipation in the battery module. This trade off will be determined by the severity of expected imbalance.

CELL BALANCING WITH PS401

The PS401 monitors all individual cell voltages, and with its programmable I/O pins, it can be programmed to control the external power transistors to bleed balancing current whenever voltage imbalance exists. It can also enable balancing only when charging if desired. A reference circuit is shown in Figure 1.


The resistor values in the above schematic can be chosen to limit the balance current to any required amount based on balancing speed vs. power consumption. PS401 firmware will control I/O1-4 to turn on the pass transistors when cell imbalance is measured on the Vcell pins, and only during charge phase if desired.

The cell balancing control could also be turned on only when the cells are near full, based on the PS401 fuel gauge. Because voltage curves are flat in the middle of the voltage vs. capacity curve, the voltage differential due to capacity imbalance is only prominent near full and near empty. To save power, cell balancing can be enabled only during charge phase, and only when the cells are almost full, entering the steep voltage curve phase. For example the transistors could be turned on only when:

- Cells are charging
- Voltage differs more than 100 mV
- Fuel gauge is more than 75% full

The PS401 can be programmed to handle all of this control with no intervention by the host system.

FIGURE 1: CELL BALANCING CIRCUIT WITH PS401

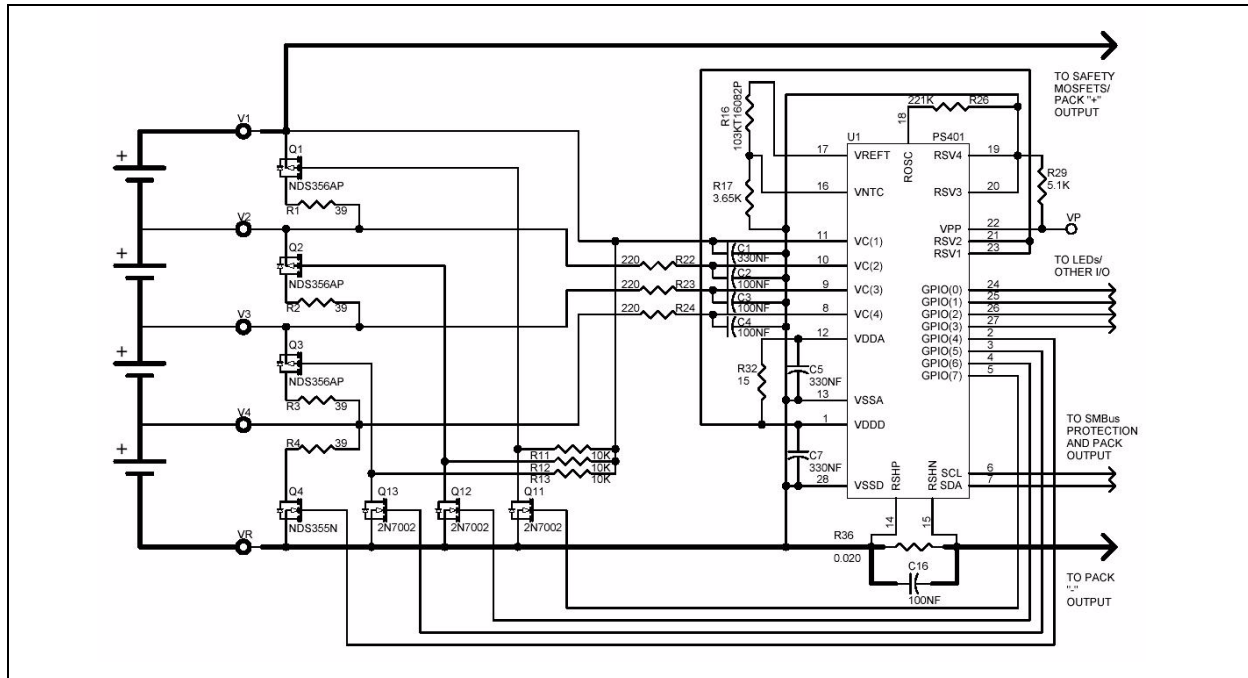

CELL BALANCING WITH EXTERNAL INTEGRATED CIRCUIT BALANCER/ PROTECTOR

Some protector circuits have built in cell balancing circuitry that will monitor voltage and drain cells without the need for external transistors. As stated before, these IC's do not have the current drain capability of external transistors, but have more capability than an ordinary IC. One such protector circuit with built in balancing is the AIC1804 from Analog Integrated Circuits. This IC has overcharge protection and cell balancing for up to four series cells. The cell balancing circuit can drain 9 mA of current. Since this function is integrated into the protector circuit, there are no other extra components needed and power consumption of the module will be less than with external transistors.

SUMMARY

- To correct small imbalances with current less than 10 mA, use a protector IC with integrated cell balancing function such as AIC1804.
- To correct larger imbalances with current on the order of 100 mA, use a battery gauge IC with built in cell balance control functions, such as Microchip PS401, with external pass transistors.
- The choice will depend on expected imbalance, and tolerable battery module power consumption.
- The capacity balance correction is equal to the balance current x time, the voltage imbalance as a function of capacity correction will vary over the battery cycle – it will be greater near full and empty.

Information contained in this publication regarding device applications and the like is intended through suggestion only and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. No representation or warranty is given and no liability is assumed by Microchip Technology Incorporated with respect to the accuracy or use of such information, or infringement of patents or other intellectual property rights arising from such use or otherwise. Use of Microchip's products as critical components in life support systems is not authorized except with express written approval by Microchip. No licenses are conveyed, implicitly or otherwise, under any intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo and PowerSmart are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

Accuron, PowerTool, SmartSensor, SmartShunt, SmartTel, PowerCal and PowerInfo are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2002, Microchip Technology Incorporated. Printed in the U.S.A., All Rights Reserved.



Printed on recycled paper.



MICROCHIP

WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200 Fax: 480-792-7277
Technical Support: 480-792-7627
Web Address: <http://www.microchip.com>

Rocky Mountain

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7966 Fax: 480-792-4338

Atlanta

3780 Mansell Road, Suite 130
Alpharetta, GA 30022
Tel: 770-640-0034 Fax: 770-640-0307

Boston

2 Lan Drive, Suite 120
Westford, MA 01886
Tel: 978-692-3848 Fax: 978-692-3821

Chicago

333 Pierce Road, Suite 180
Itasca, IL 60143
Tel: 630-285-0071 Fax: 630-285-0075

Dallas

4570 Westgrove Drive, Suite 160
Addison, TX 75001
Tel: 972-818-7423 Fax: 972-818-2924

Detroit

Tri-Atria Office Building
32255 Northwestern Highway, Suite 190
Farmington Hills, MI 48334
Tel: 248-538-2250 Fax: 248-538-2260

Kokomo

2767 S. Albright Road
Kokomo, Indiana 46902
Tel: 765-864-8360 Fax: 765-864-8387

Los Angeles

18201 Von Karman, Suite 1090
Irvine, CA 92612
Tel: 949-263-1888 Fax: 949-263-1338

San Jose

Microchip Technology Inc.
2107 North First Street, Suite 590
San Jose, CA 95131
Tel: 408-436-7950 Fax: 408-436-7955

Toronto

6285 Northam Drive, Suite 108
Mississauga, Ontario L4V 1X5, Canada
Tel: 905-673-0699 Fax: 905-673-6509

ASIA/PACIFIC

Australia

Microchip Technology Australia Pty Ltd
Suite 22, 41 Rawson Street
Epping 2121, NSW
Australia
Tel: 61-2-9868-6733 Fax: 61-2-9868-6755

China - Beijing

Microchip Technology Consulting (Shanghai)
Co., Ltd., Beijing Liaison Office
Unit 915
Bei Hai Wan Tai Bldg.
No. 6 Chaoyangmen Beidajie
Beijing, 100027, No. China
Tel: 86-10-85282100 Fax: 86-10-85282104

China - Chengdu

Microchip Technology Consulting (Shanghai)
Co., Ltd., Chengdu Liaison Office
Rm. 2401-2402, 24th Floor,
Ming Xing Financial Tower
No. 88 TIDU Street
Chengdu 610016, China
Tel: 86-28-86766200 Fax: 86-28-86766599

China - Fuzhou

Microchip Technology Consulting (Shanghai)
Co., Ltd., Fuzhou Liaison Office
Unit 28F, World Trade Plaza
No. 71 Wusi Road
Fuzhou 350001, China
Tel: 86-591-7503506 Fax: 86-591-7503521

China - Hong Kong SAR

Microchip Technology Hongkong Ltd.
Unit 901-6, Tower 2, Metroplaza
223 Hing Fong Road
Kwai Fong, N.T., Hong Kong
Tel: 852-2401-1200 Fax: 852-2401-3431

China - Shanghai

Microchip Technology Consulting (Shanghai)
Co., Ltd.
Room 701, Bldg. B
Far East International Plaza
No. 317 Xian Xia Road
Shanghai, 200051
Tel: 86-21-6275-5700 Fax: 86-21-6275-5060

China - Shenzhen

Microchip Technology Consulting (Shanghai)
Co., Ltd., Shenzhen Liaison Office
Rm. 1812, 18/F, Building A, United Plaza
No. 5022 Binhe Road, Futian District
Shenzhen 518033, China
Tel: 86-755-82901380 Fax: 86-755-82966626

China - Qingdao

Rm. B503, Fullhope Plaza,
No. 12 Hong Kong Central Rd.
Qingdao 266071, China
Tel: 86-532-5027355 Fax: 86-532-5027205

India

Microchip Technology Inc.
India Liaison Office
Divyasree Chambers
1 Floor, Wing A (A3/A4)
No. 11, O'Shaughnessey Road
Bangalore, 560 025, India
Tel: 91-80-2290061 Fax: 91-80-2290062

Japan

Microchip Technology Japan K.K.
Benex S-1 6F
3-18-20, Shinyokohama
Kohoku-Ku, Yokohama-shi
Kanagawa, 222-0033, Japan
Tel: 81-45-471-6166 Fax: 81-45-471-6122

Korea

Microchip Technology Korea
168-1, Youngbo Bldg. 3 Floor
Samsung-Dong, Kangnam-Ku
Seoul, Korea 135-882
Tel: 82-2-554-7200 Fax: 82-2-558-5934

Singapore

Microchip Technology Singapore Pte Ltd.
200 Middle Road
#07-02 Prime Centre
Singapore, 188980
Tel: 65-6334-8870 Fax: 65-6334-8850

Taiwan

Microchip Technology (Barbados) Inc.,
Taiwan Branch
11F-3, No. 207
Tung Hua North Road
Taipei, 105, Taiwan
Tel: 886-2-2717-7175 Fax: 886-2-2545-0139

EUROPE

Austria

Microchip Technology Austria GmbH
Durisolstrasse 2
A-4600 Wels
Austria
Tel: 43-7242-2244-399
Fax: 43-7242-2244-393

Denmark

Microchip Technology Nordic ApS
Regus Business Centre
Lautrup høj 1-3
Ballerup DK-2750 Denmark
Tel: 45 4420 9895 Fax: 45 4420 9910

France

Microchip Technology SARL
Parc d'Activite du Moulin de Massy
43 Rue du Saule Trapu
Batiment A - 1er Etage
91300 Massy, France
Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79

Germany

Microchip Technology GmbH
Steinheilstrasse 10
D-85737 Ismaning, Germany
Tel: 49-89-627-144 0 Fax: 49-89-627-144-44

Italy

Microchip Technology SRL
Centro Direzionale Colleoni
Palazzo Taurus 1 V. Le Colleoni 1
20041 Agrate Brianza
Milan, Italy
Tel: 39-039-65791-1 Fax: 39-039-6899883

United Kingdom

Microchip Ltd.
505 Eskdale Road
Winkersley Triangle
Wokingham
Berkshire, England RG41 5TU
Tel: 44 118 921 5869 Fax: 44-118 921-5820

12/05/02