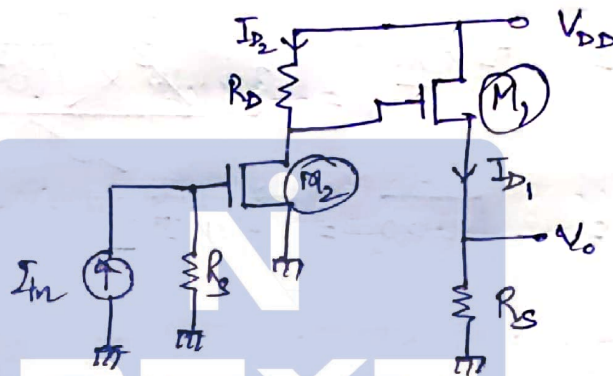


# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q-1 (a) | Given circuit shows a  
shunt - shunt feedback or voltage - shunt feedback.

Decoupled circuit:-



Now For  $M_2$ :  $V_{GS2} = I_{in} R_S$

& For  $M_1$ :  $V_{GS1} = (V_{DD} - I_{D2} R_D) - V_o$


&  $V_o = I_{D1} R_S$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.

( Specimen Answer Booklet - For Practice Purpose Only)

Q.1(b) | Turning given circuit into Laplace domain:-

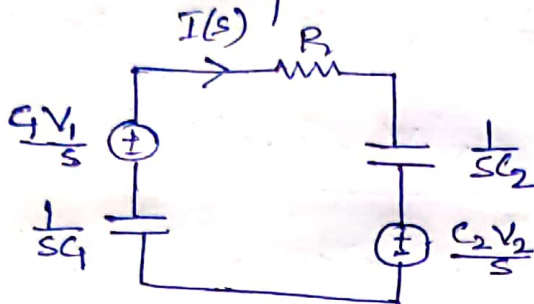

Now Applying KVL:-

$$\frac{I(s)}{sC_1} - \frac{C_1 V_1}{s} + RI(s) + \frac{I(s)}{sC_2} + \frac{C_2 V_2}{s} = 0$$

$$\Rightarrow I(s) \left[ \frac{1}{sC_1} + \frac{1}{sC_2} + R \right] = \frac{C_1 V_1 - C_2 V_2}{s}$$

$$\Rightarrow I(s) \left[ \frac{sC_1 C_2 R + C_2 + C_1}{sC_1 C_2} \right] = \frac{C_1 V_1 - C_2 V_2}{s}$$

$$\Rightarrow I(s) = \frac{[C_1 V_1 - C_2 V_2] C_1 C_2}{C_1 + C_2 + s C_1 C_2 R}$$

$$= \frac{[C_1 V_1 - C_2 V_2]}{R \left[ s + \frac{C_1 + C_2}{R C_1 C_2} \right]}$$

Taking inverse Laplace transform:-

$$i(t) = \frac{C_1 V_1 - C_2 V_2}{R} \cdot e^{-\frac{(C_1 + C_2)t}{R C_1 C_2}} \cdot u(t)$$

Now total energy absorbed by resistor

$$= \int_0^{\infty} \left[ \frac{K}{R} \cdot e^{-\frac{(C_1 + C_2)t}{R C_1 C_2}} \right]^2 \cdot R \cdot dt$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$= \frac{K^2}{R} \cdot \int_0^{\infty} e^{-2(\text{Ceq}/R)t} dt$$
$$= \frac{K^2}{R} \cdot \frac{R}{-2\text{Ceq}} \cdot \left[ e^{-2(\text{Ceq}/R)t} \right]_0^{\infty}$$

$$\boxed{\text{Energy} = \frac{K^2}{2\text{Ceq}}}$$

where  $K = C_1 V_1 - C_2 V_2$   
&  $\text{Ceq} = \frac{C_1 C_2}{C_1 + C_2}$

Thus energy absorbed by R is  
independent of the value of R.

Q.1(c)  $\vec{H} = 2 \cos(\omega t - 3y) \hat{a}_z$

Given  $\sigma = 0$ ;  $\mu_r = 2$ ;  $\epsilon_r = 5$

We know that for a medium  
speed  $(v) = \frac{\omega}{\beta} = \frac{1}{\sqrt{\mu\epsilon}}$

$$\text{or } \frac{\omega}{3} = \frac{1}{\sqrt{\mu_r \epsilon_r} \cdot \mu_0 \epsilon_0} = \frac{3 \times 10^8}{\sqrt{2 \times 5}}$$

$$\Rightarrow \omega = \frac{9 \times 10^8}{\sqrt{10}} \text{ rad/s}$$

$$\Rightarrow \boxed{\omega = 2.85 \times 10^8 \text{ rad/s}}$$

Now  $\vec{E} = E_0 \cos(\omega t - 3y) \cdot \hat{a}_E$

deduced from the form of  $\vec{H}$ .

where  $\hat{a}_E = \hat{a}_k \times \hat{a}_H = \hat{a}_y \times \hat{a}_z = \hat{a}_x$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\& \boxed{\frac{E_0}{H_0} = \eta} \quad \text{where } \eta = \sqrt{\frac{\mu}{\epsilon}} = \sqrt{\frac{\mu_r}{\epsilon_r}} \times 120\pi \Omega$$

$$\Rightarrow E_0 = 238.43 \times 2 \text{ V/m} \quad \eta = 238.43 \Omega$$

$$\boxed{E_0 = 476.86 \text{ V/m}}$$

$$\text{Thus } \boxed{\vec{E} = 476.86 \cos(2.85 \times 10^8 t - 3y) \hat{a}_y \text{ V/m}}$$

Q.1(d)

Since we need causal sequence  $\Rightarrow$  ROC is of the form  $|z| > z_0$

$$\text{Now } X(z) = \frac{1 + 2z^{-1}}{1 - 2z^{-1} + 4z^{-2}} \times \frac{z^2}{z^2}$$

$$= \frac{z(z+2)}{z^2 - 2z + 4}$$

$$\text{or } \frac{X(z)}{z} = \frac{z+2}{z^2 - 2z + 4}$$

$$\frac{X(z)}{z} = \frac{z+2}{(z-1-\sqrt{3}j)(z-1+\sqrt{3}j)}$$

$$\begin{aligned} \text{roots} &= \frac{2 \pm \sqrt{4-16}}{2} \\ &= \frac{2 \pm 2\sqrt{3}j}{2} \\ &= 1 \pm \sqrt{3}j \end{aligned}$$

$$\text{Now } \frac{X(z)}{z} = \frac{A}{z-1-\sqrt{3}j} + \frac{B}{z-1+\sqrt{3}j}$$

where A & B are constants.

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
(Specimen Answer Booklet - For Practice Purpose Only)

$$A = (z - 1 - \sqrt{3}j) \cdot \frac{X(z)}{z} \Big|_{z=1+\sqrt{3}j} = \frac{3 + \sqrt{3}j}{2\sqrt{3}j} = \frac{\sqrt{3} + j}{2j}$$

$$B = (z - 1 + \sqrt{3}j) \cdot \frac{X(z)}{z} \Big|_{z=1-\sqrt{3}j} = \frac{3 - \sqrt{3}j}{-2\sqrt{3}j} = \frac{\sqrt{3} - j}{-2j}$$

$$\Rightarrow \frac{X(z)}{z} = \frac{\sqrt{3} + j}{2j} \cdot \frac{1}{z - 1 - \sqrt{3}j} - \frac{\sqrt{3} - j}{2j} \cdot \frac{1}{z - 1 + \sqrt{3}j}$$

$$\text{or } X(z) = \frac{\sqrt{3} + j}{2j} \cdot \frac{1}{1 - (1 + \sqrt{3}j)z^{-1}} - \frac{\sqrt{3} - j}{2j} \cdot \frac{1}{1 - (1 - \sqrt{3}j)z^{-1}}$$

Taking inverse Z transform, knowing that  $\left\{ \frac{1}{1 - az^{-1}} \right\} \xrightarrow{ZT^{-1}} a^n u(n)$

$$\Rightarrow \cancel{X(z)} \quad x(n) = \frac{\sqrt{3} + j}{2j} (1 + \sqrt{3}j)^n u(n) - \frac{\sqrt{3} - j}{2j} (1 - \sqrt{3}j)^n u(n)$$

$$\text{Now } \frac{\sqrt{3}}{2} + \frac{1}{2}j = e^{j\pi/6} ; \quad \frac{\sqrt{3}}{2} - \frac{1}{2}j = e^{-j\pi/6}$$

$$\frac{1}{2} + \frac{\sqrt{3}}{2}j = e^{j\pi/3} ; \quad \frac{1}{2} - \frac{\sqrt{3}}{2}j = e^{-j\pi/3}$$

$$\text{so; } x(n) = u(n) \left[ \frac{e^{j\pi/6}}{j} \cdot 2 \cdot e^{jn\pi/3} - \frac{e^{-j\pi/6}}{j} \cdot 2 \cdot e^{-jn\pi/3} \right]$$

$$= 2^n u(n) \cdot \left[ \frac{e^{j(\frac{n\pi}{3} + \frac{\pi}{6})} - e^{-j(\frac{n\pi}{3} + \frac{\pi}{6})}}{2j} \right] \times 2$$

$$x(n) = 2^{n+1} \sin\left(\frac{n\pi}{3} + \frac{\pi}{6}\right) u(n)$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q(1)(c) For right half:-

$$V_2 = I_2 \times 20\Omega$$

$$\text{Now } V_1 = - \frac{I_2 \times 20}{2}$$

$$V_1 = -I_2 \times 10$$

using turns ratio  
& dot convention

$$\text{Now } 120 = (4 - 6j) I_1 - I_2 \times 10$$

$$\text{But by turns ratio } I_2 = -\frac{I_1}{2}$$

$$\Rightarrow 120 = (4 - 6j) I_1 + \frac{I_1}{2} \times 10$$

$$120 = I_1 (4 - 6j + 5)$$

$$120 = +I_1 (9 + 6j)$$

$$\therefore I_1 = \frac{120}{9 + 6j} = \boxed{19.73 / 99.5^\circ \text{ A}}$$

$$\text{Now } I_2 = \frac{I_1}{2}$$

$$I_1 = 11.1 / -33.7^\circ \text{ A}$$

$$\therefore I_2 = -\frac{I_1}{2} =$$

$$\boxed{5.55 / 146.3^\circ \text{ A}}$$

$$\therefore V_o = 20 \times I_2 \Rightarrow \boxed{111 / 146.3^\circ \text{ A}}$$

Now complex power supplied by

$$\text{source} = V_{\text{rms}} \times I_{\text{rms}}^* = 120 \times 11.1 / 33.7^\circ$$

$$\boxed{S = 1332 / 33.7^\circ \text{ VA}}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q.5(a)

Considering the Thvenin equivalent



$$\text{Now Case 1:- } V_s = (R_{th} + 5) \times 4A$$

$$\text{Case 2:- } V_s = (R_{th} + 20) \times 2A$$

$$\Rightarrow \frac{R_{th} + 5}{R_{th} + 20} = \frac{1}{2}$$

$$2R_{th} + 10 = R_{th} + 20 \Rightarrow R_{th} = 10 \Omega$$

$$\text{Now } V_s = (10 + 5) \times 4 = 60V$$

(i) For max power transfer;  
using theorem  $R_L = R_{th}$

$$\Rightarrow R_L = 10 \Omega$$

(ii) Max power delivered to load

$$= \frac{V_{th}^2}{4 \cdot R_{th}} = \frac{(60)^2}{4 \times 10} = 90W$$

(iii) When delivering 50W to load

$\Rightarrow$  Let load is  $R \Omega$

$$V \text{ voltage} = V \times \frac{R}{R+10}$$

$$\& \text{ power} = \left( \frac{V \times R}{R+10} \right)^2 \times \frac{1}{R} = \frac{3600R}{(R+10)^2}$$

$$\Rightarrow \frac{3600R}{(R+10)^2} = 50 \Rightarrow R^2 + 20R + 100 = R \times 72$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
(Specimen Answer Booklet - For Practice Purpose Only)

~~$R^2 + 52R + 100 = 0 \Rightarrow R =$~~

$$R^2 - 52R + 100 = 0 \Rightarrow R = \frac{52 \pm 48}{2} = 50 \Omega \text{ or } 2 \Omega$$

Now total power from source :-

$$\frac{(60)^2}{10+50} = 60 \text{ W}$$

$$\text{or } \frac{(60)^2}{10+2} = 300 \text{ W}$$

Power delivered to load = 50 W

$\Rightarrow$  Power transfer efficiency

$$\frac{50}{60} \times 100 = \boxed{83.33\%}$$

$$\frac{50}{300} \times 100 = \boxed{16.67\%}$$

Q-5(b)

Now we know that

$$e^{-j\omega_0 t} \cdot x(t) \xleftrightarrow{FT} X(\omega + \omega_0)$$

$$\Rightarrow \left[ \frac{e^{j\omega_0 t} + e^{-j\omega_0 t}}{2} \right] x(t) \xleftrightarrow{FT} \frac{1}{2} \left[ X(\omega + \omega_0) + X(\omega - \omega_0) \right]$$


So, If  $y(t) \xleftrightarrow{FT} Y(\omega)$

then  $y(t) \cos \omega_0 t \xleftrightarrow{FT} \frac{1}{2} \left[ Y(\omega + \omega_0) + Y(\omega - \omega_0) \right]$


①

Now

$$y'(t) =$$

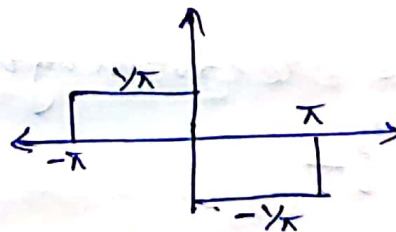

$$y''(t) =$$

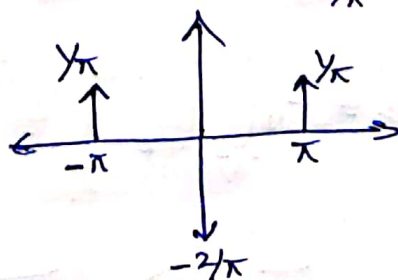



# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\text{Now } y''(t) = \frac{1}{\pi} \delta(t+\pi) - \frac{2}{\pi} \delta(t) + \frac{1}{\pi} \delta(t-\pi)$$

$$\Rightarrow (j\omega)^2 \cdot Y(\omega) = \frac{1}{\pi} [e^{j\omega\pi} + e^{-j\omega\pi}] - \frac{2}{\pi}$$

$$\text{or } Y(\omega) = \frac{1}{\pi\omega^2(-1)} [2\cos\pi\omega - 2]$$

$$Y(\omega) = \frac{2}{\pi\omega^2} [1 - \cos\pi\omega]$$

$$\Rightarrow X(\omega) = \frac{1}{2} \left[ \frac{2}{\pi(\omega+10)^2} [1 - \cos(\pi\omega+10\pi)] + \frac{2}{\pi(\omega-10)^2} [1 - \cos(\pi\omega-10\pi)] \right]$$

From (1)

$$\text{But } \cos(2\pi+\theta) = \cos(2\pi-\theta) = \cos(\theta-2\pi) = \cos\theta$$

$$\Rightarrow X(\omega) = \frac{1}{\pi} \left[ \frac{1 - \cos\omega\pi}{(\omega+10)^2} + \frac{1 - \cos\omega\pi}{(\omega-10)^2} \right]$$


Q.5(c) Poynting theorem states that the flow of energy in a flowing/travelling electromagnetic wave is given by :-

$$\oint_S (\vec{E} \times \vec{H}) \cdot d\vec{S} = -\frac{d}{dt} \int_V \left( \frac{\epsilon E^2}{2} + \frac{\mu H^2}{2} \right) dv - \int_V \sigma E^2 dv$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q.5(d)

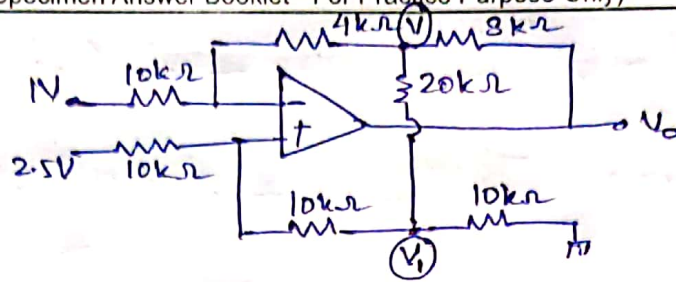

Now using virtual ground & other op-amp properties, we know that current doesn't enter i/p terminals.

$$\text{Now } \cancel{(2.5 - V_1)} \times \frac{10}{10+10} = \cancel{(1 - V)} \times$$

At node with voltage  $V_1$ ; using KCL: -

$$\frac{V-1}{14k\Omega} + \frac{V-V_1}{20k\Omega} + \frac{V-V_0}{8k\Omega} = 0 \quad \text{--- (I)}$$

$$\frac{V_1-2.5}{20k\Omega} + \frac{V_1-V}{20k\Omega} + \frac{V_1}{10k\Omega} = 0 \quad \text{--- (II)}$$

$$\& \quad 2.5 - \frac{2.5 - V_1}{20k\Omega} \times 10k\Omega = 1 - \frac{1 - V}{14k\Omega} \times 10k\Omega$$

$$1.5 = \frac{2.5 - V_1}{2} - \frac{(1 - V) \times 5}{7}$$

$$\Rightarrow \frac{V_1}{2} = \left( \frac{2.5}{2} - 1.5 \right) - \frac{5}{7} + \frac{5V}{7}$$

$$\frac{V_1}{2} = \frac{5V}{7} - \frac{27}{28} \Rightarrow$$

$$\boxed{V_1 = \frac{10V}{7} - \frac{27}{14}}$$

Now from (II)  $V_1 \left( \frac{1}{20k\Omega} + \frac{1}{20k\Omega} + \frac{1}{10k\Omega} \right) = \frac{2.5}{20k\Omega} + \frac{V}{20k\Omega}$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\Rightarrow \frac{V_1}{5} = \frac{1}{8} + \frac{V}{20} \Rightarrow \frac{1}{5} \left( \frac{10V}{7} - \frac{27}{14} \right) = \frac{1}{8} + \frac{V}{20}$$

$$\frac{2V}{7} - \frac{27}{70} = \frac{1}{8} + \frac{V}{20} \Rightarrow V \left( \frac{2}{7} - \frac{1}{20} \right) = \frac{27}{70} + \frac{1}{8}$$

$$V \times \frac{33}{140} = \frac{143}{280}$$

$$\text{or } \boxed{V = \frac{13}{6} V} \Rightarrow \boxed{V_1 = \frac{7}{6} V}$$

$\therefore$  Putting into (1):—


$$\frac{13/6 - 1}{14} + \frac{13/6 - 7/6}{20} + \frac{13/6 - V_0}{8} = 0$$

$$\frac{1}{12} + \frac{1}{20} + \frac{13}{48} = \frac{V_0}{8}$$

$$\Rightarrow \boxed{V_0 = \frac{97}{30} V} \text{ or } \boxed{V_0 = 3.23 V}$$

Q.1(e)

Apply mesh analysis:—

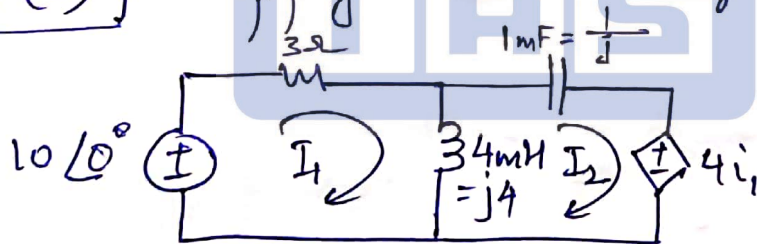

$$\text{Now } 10 = 3I_1 + j4(I_1 - I_2) \quad \text{--- (1)}$$

$$\frac{1}{j} I_2 + 4I_1 + j4(I_2 - I_1) = 0 \quad \text{--- (2)}$$

$$\text{From (1) we get } (3 + j4)I_1 - j4I_2 = 10$$

$$\text{From (2) we get } 3jI_2 + (4 - 4j)I_1 = 0$$

$$\Rightarrow I_2 = -\frac{4 - 4j}{3j} I_1$$

$$I_2 = \frac{4}{3}(1 + j)I_1 \quad \text{--- (3)}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.

( Specimen Answer Booklet - For Practice Purpose Only)

$$\rightarrow (3+4j) I_1 - j4 \left( \frac{4}{3} + \frac{4j}{3} \right) I_1 = 10$$

$$\rightarrow I_1 \left[ 3+4j + \frac{16}{3} - \frac{16j}{3} \right] = 10$$

$$I_1 = \frac{10}{\frac{25}{3} - \frac{4j}{3}} = (1.17 + 0.19j) \text{ A}$$

$$\text{or } i_1(t) = 1.185 \cos(10^3 t + 9.1^\circ) \text{ A}$$

$$\& I_2 = \frac{4}{3} (1+j) I_1 = 2.234 \angle 54.1^\circ \text{ A}$$

$$\text{or } i_2(t) = 2.234 \cos(10^3 t + 54.1^\circ) \text{ A}$$

N  
NEXT  
DAS

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q.4(a) Given  $y(n) - y(n-1) = x(n) + x(n-1)$

Taking z transform: -

$$Y(z) \cdot [1 - z^{-1}] = X(z) [1 + z^{-1}]$$

$$\Rightarrow \frac{Y(z)}{X(z)} = \frac{1 + z^{-1}}{1 - z^{-1}} = \boxed{\frac{z+1}{z-1}}$$

Now for the causal system: -

$$H(z) = \frac{1}{1 - z^{-1}} + \frac{z^{-1}}{1 - z^{-1}}$$

Now if  $\frac{1}{1 - z^{-1}} \xleftrightarrow{zT^{-1}} u(n)$

~~also~~ we know by property that

$$u(n-1) \xleftrightarrow{zT} z^{-1} \{ zT(u(n)) \} = \frac{z^{-1}}{1 - z^{-1}}$$

$$\Rightarrow zT^{-1} \{ H(z) \} = u(n) + u(n-1)$$

$$\text{or } \boxed{h(n) = u(n) + u(n-1)}$$

(ii) Now  $H(z) = \frac{1 + z^{-1}}{(1 - z^{-1})}$  &  $X(z) = \frac{1}{1 - z^{-1}}$

$$\Rightarrow Y(z) = \frac{(1 + z^{-1})}{(1 - z^{-1})^2}$$

$$\text{or } Y(z) = \frac{z(z+1)}{(z-1)^2}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\text{Now } \frac{Y(z)}{z} = \frac{z+1}{(z-1)^2} =$$

$$Y(z) = \frac{1}{(1-z^{-1})^2} + \frac{z^{-1}}{(1-z^{-1})^2}$$

$$\text{Now we know that } nu(n) \xrightarrow{zT} \frac{z^{-1}}{(1-z^{-1})^2}$$

$$\& x(n+1) \longrightarrow z \cdot X(z)$$

$$\Rightarrow z \cdot \frac{z^{-1}}{(1-z^{-1})^2} \xrightarrow{zT^{-1}} (n+1)u(n+1)$$

$$\Rightarrow \boxed{y(n) = (n+1)u(n+1) + nu(n)}$$

$$\text{Now for } x(n) = 2^{-n}u(n); X(z) = \frac{1}{1-\frac{1}{2}z^{-1}}$$

or  $(\frac{1}{2})^n u(n)$

$$\Rightarrow Y(z) = \frac{1+z^{-1}}{(1-z^{-1})(1-\frac{1}{2}z^{-1})} = \frac{z(z+1)}{(z-1)(z-\frac{1}{2})}$$

$$\text{or } \frac{Y(z)}{z} = \frac{z+1}{(z-1)(z-\frac{1}{2})} = \frac{A}{z-1} + \frac{B}{z-\frac{1}{2}}$$

$$\text{Now } A = \left. \frac{(z-1)Y(z)}{z} \right|_{z=1} = \frac{2}{\frac{1}{2}} = 4$$

$$B = \left. \frac{(z-\frac{1}{2})Y(z)}{z} \right|_{z=\frac{1}{2}} = \frac{\frac{3}{2}}{-\frac{1}{2}} = -3$$

$$\Rightarrow \frac{Y(z)}{z} = \frac{4}{z-1} - \frac{3}{z-\frac{1}{2}} \Rightarrow Y(z) = \frac{4}{1-z^{-1}} - \frac{3}{1-\frac{1}{2}z^{-1}}$$

$$\text{Taking IFT: } \boxed{y(n) = 4u(n) - 3\left(\frac{1}{2}\right)^n u(n)}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q.4(b)

For the circuit in DC mode:-

$$I_E = 10 \text{ mA}; V_{CC} = 15 \text{ V}; V_{BE} = 0.7 \text{ V}$$

$$\beta = 100 \text{ V} \& V_E = V_{CE} = 5 \text{ V}$$

$$\Rightarrow I_E = \frac{5 \text{ V}}{R_E} = \frac{(100+1)}{100} \times I_C = \frac{101}{100} \times 10 \text{ mA}$$

$$\Rightarrow R_E = \frac{5 \times 100}{101 \times 10 \text{ mA}} = \boxed{495 \Omega}$$

Now  $V_{CE} = V_E = 5 \text{ V} \Rightarrow$  voltage across

$$R_C = 5 \text{ V}$$

$$\Rightarrow 10 \text{ mA} \times R_C = 5 \text{ V}$$

$$\text{or } \boxed{R_C = 500 \Omega}$$

$$\text{Now } V_{Th} = 15 \times \frac{R_2}{R_1 + R_2}$$

$$\& R_{Th} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{Now } V_{Th} - I_B R_{Th} - 0.7 = V_E$$

$$\frac{15 R_2}{R_1 + R_2} - 1 \mu\text{A} \times \frac{R_1 R_2}{R_1 + R_2} = 5 + 0.7$$

$$\text{or } \frac{R_2}{R_1 + R_2} [15 - R_1 \times 10^{-6}] = 5.7$$

$$\text{Let's choose } \boxed{R_1 = \cancel{10 \text{ M}\Omega} 5 \text{ M}\Omega}$$

$$\Rightarrow \frac{R_2}{5 \times 10^6 + R_2} \times (15 - \frac{5}{10}) = 5.7$$


$$\text{or } 1 + \frac{5 \times 10^6}{R_2} = \frac{10}{5.7}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\Rightarrow \frac{5 \times 10^6}{R_2} = \frac{4.3}{5.7} \Rightarrow \boxed{R_2 = 6.63 \text{ M}\Omega}$$

Now for small signal gain:-

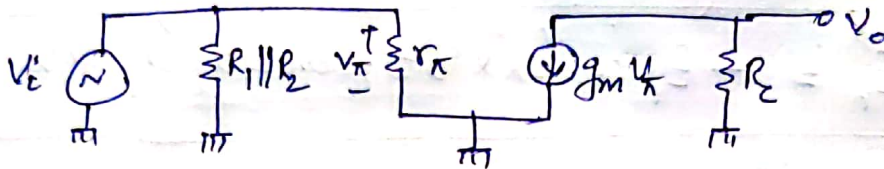

$$\text{Now } V_o = -g_m V_\pi R_c \text{ where } V_\pi = V_i$$

$$\frac{V_o}{V_i} = -g_m R_c$$

$$\text{Now } g_m = \frac{I_c}{V_T} = \frac{10 \text{ mA}}{26 \text{ mV}} = \frac{5}{13}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{5}{13} \times 500 = \boxed{-192.31}$$

Q.4 (c)

$$\omega = 2\pi \times 10^6 \text{ rad/s}; \sigma \gg \omega \epsilon$$

$$\Rightarrow \eta = \sqrt{\frac{j\omega \mu}{\sigma}} = \sqrt{\frac{2\pi \times 10^6 \times 4\pi \times 10^{-7}}{5.2 \times 10^7}} \angle 45^\circ \Omega$$

$$\boxed{\eta = 3.7 \times 10^{-4} \angle 45^\circ \Omega}$$

Now incident wave  $\Rightarrow$

$$\vec{E} = E_i \cos(\omega t - \beta x) \hat{a}_y \text{ V/m}$$

$$\text{Here } \omega = 2\pi \times 10^6 \text{ rad/s} \text{ \& } \beta = \frac{\omega}{3 \times 10^8} \text{ rad/m}$$

$$f = 0.021 \text{ rad/m}$$

$$\text{So, } \boxed{\vec{E}_i = E_i \cos(2\pi \times 10^6 t - 0.021 x) \hat{a}_y \text{ V/m}}$$

$$\text{Now given } \eta_2 = 3.7 \times 10^{-4} \angle 45^\circ \text{ \& } \eta_1 = 120 \pi$$

$$\Gamma = \frac{(\eta_2 - \eta_1)}{\eta_2 + \eta_1}$$



# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\text{But } \eta_2 \ll \eta_1 \Rightarrow \Gamma \approx -1$$

$$\text{So, } E_r = -1 \times E_i$$

& travelling wave in  $-x$  direction.

$$\Rightarrow \vec{E}_r = -E_i \cos(2\pi \times 10^6 t + 0.021x) \hat{a}_y \text{ V/m}$$

For transmitted wave

$$\tau = \frac{2\eta_2}{\eta_1 + \eta_2} = \frac{2 \times 3.7 \times 10^{-4} / 45^\circ}{120\pi}$$

$$\tau = 2 \times 10^{-6} / 45^\circ$$

$$\Rightarrow E_t = 2 \times 10^{-6} E_i \text{ \& } \beta_2 = \sqrt{\pi f \mu \sigma}$$

$$= \sqrt{\pi \times 10^6 \times \frac{4\pi}{10^7} \times 5.2 \times 10^7}$$
$$= 15132 \text{ m}^{-1}$$

$$\Rightarrow \vec{E}_t = 2 \times 10^{-6} E_i \cos(2\pi \times 10^6 t - 15132x) \hat{a}_y \text{ V/m}$$

However there is also  $\alpha = 15132 \text{ m}^{-1}$

$$\text{So, } \vec{E}_t = 2 \times 10^{-6} E_i e^{-15132x} \cos(2\pi \times 10^6 t - 15132x) \hat{a}_y \text{ V/m}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q.7(a) Now in steady state?


capacitors are open & inductors are short

$$\Rightarrow i = \frac{10}{10} = 1A$$

$$\Rightarrow Li(0^-) = 1V$$

$$\& v(0^-) = 6i = 6V$$

Moving to Laplace domain?

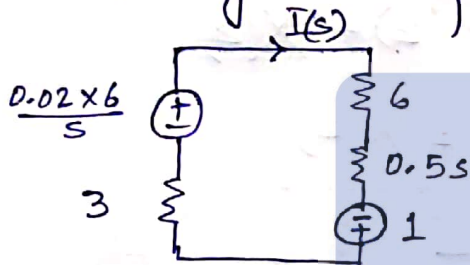

Using KVL:-

$$\frac{0.12}{s} - 6I(s) - 0.5sI(s) + 1 - 3I(s) = 0$$

$$I(s) [-6 - 0.5s - 3] + 1 + \frac{0.12}{s} = 0$$

$$\Rightarrow I(s) = \frac{1 + \frac{0.12}{s}}{9 + 0.5s} = \frac{0.12 + s}{s(0.5s + 9)}$$

$$\text{or } I(s) = \frac{2(s + 0.12)}{s(s + 18)} = \frac{A}{s} + \frac{B}{s + 18}$$

$$\text{Now } A = s \cdot I(s) \Big|_{s=0} = \frac{2 \times 0.12}{18} = \frac{1}{75}$$

$$B = (s + 18)I(s) \Big|_{s=-18} = \frac{2 \times (-17.88)}{-18} = \frac{149}{75}$$

$$\text{Now } I(s) = \frac{1}{75} \cdot \frac{1}{s} + \frac{149}{75} \cdot \frac{1}{s + 18}$$

$$\text{or } i(t) = \frac{1}{75} \cdot u(t) + \frac{149}{75} \cdot e^{-18t} u(t)$$

$$i(t) = \frac{1}{75} [1 + 149e^{-18t}] u(t)$$

$$\text{Now } V(s) = \frac{0.12}{s} - 3I(s)$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$V(s) = \frac{2}{25} \cdot \frac{1}{s} - \frac{149}{25} \cdot \frac{1}{s+18}$$

$$\Rightarrow v(t) = \frac{2}{25} u(t) - \frac{149}{25} e^{-18t} u(t)$$

$$v(t) = \frac{1}{25} [2 - 149 e^{-18t}] u(t)$$

Q.7(b)

Now taking z transform:-

$$Y(z) = 0.95 z^{-1} Y(z) + X(z)$$

$$\Rightarrow Y(z) \cdot [1 - 0.95 z^{-1}] = X(z)$$

$$\text{or } \frac{Y(z)}{X(z)} = \frac{1}{1 - 0.95 z^{-1}} \quad \text{--- (1)}$$

$$\text{For } x(n) = \cos\left(\frac{\pi n}{20} - \frac{\pi}{2}\right) u(n)$$

$$= \sin\left(\frac{\pi n}{20}\right) u(n)$$

$$= \frac{1}{2j} [e^{j\pi n/20} - e^{-j\pi n/20}] u(n)$$

$$\text{Now } X(z) = \frac{1}{2j} \left[ \frac{1}{1 - (e^{j\pi/20}) z^{-1}} - \frac{1}{1 - (e^{-j\pi/20}) z^{-1}} \right]$$

Now using (1) :-

$$Y(z) = \frac{1}{(1 - 0.95 z^{-1})} \cdot \frac{1}{2j} \left[ \frac{1}{1 - e^{j\pi/20} z^{-1}} - \frac{1}{1 - e^{-j\pi/20} z^{-1}} \right]$$

Now by final value theorem:-

$$y_{ss}(n) = \lim_{z \rightarrow 1} (z-1) \cdot Y(z)$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\lim_{z \rightarrow 1} (z-1) Y(z) = 0 \quad \text{or} \quad \boxed{y_{ss}(n) = 0}$$

$$\begin{aligned} Y(z) &= \frac{1}{2j} \cdot \frac{z}{z-0.95} \cdot \left[ \frac{z}{z-e^{j\pi/20}} - \frac{z}{z-e^{-j\pi/20}} \right] \\ &= \frac{1}{2j} \cdot \frac{z}{z-0.95} \cdot \left[ \frac{z - z \cdot e^{-j\pi/20}}{(z-e^{j\pi/20})(z-e^{-j\pi/20})} - \frac{z - z \cdot e^{j\pi/20}}{(z-e^{j\pi/20})(z-e^{-j\pi/20})} \right] \\ &= \frac{1}{2j} \cdot \frac{z^2}{z-0.95} \cdot \left[ \frac{e^{j\pi/20} - e^{-j\pi/20}}{z^2 + 1 - z(e^{j\pi/20} + e^{-j\pi/20})} \right] \end{aligned}$$

Let  $\frac{\pi}{20} = \omega_0$  for calculation

$$\Rightarrow Y(z) = \frac{z^2}{z-0.95} \left[ \frac{\sin \omega_0}{z^2 - 2z \cos \omega_0 + 1} \right]$$

$$\Rightarrow \frac{Y(z)}{z} = \frac{z \sin \omega_0}{(z-0.95)(z^2 - 2z \cos \omega_0 + 1)}$$

$$\begin{aligned} \text{Let } \frac{Y(z)}{z} &= \frac{A}{z-0.95} + \frac{Bz+C}{z^2 - 2z \cos \omega_0 + 1} \\ &= \frac{A(z^2 - 2z \cos \omega_0 + 1) + Bz^2 - Bz \cdot 0.95 + C(z - 0.95)}{(z-0.95)(z^2 - 2z \cos \omega_0 + 1)} \end{aligned}$$

Now  $A+B=0$

$$-2 \cos \omega_0 A - B \times 0.95 + C = \sin \omega_0$$

$$\& A - C \times 0.95 = 0$$

$$\Rightarrow B = -A \quad \& \quad C = \frac{A}{0.95}$$

$$\Rightarrow -2 \cos \omega_0 A + 0.95 A + \frac{A}{0.95} = \sin \omega_0$$

$$\Rightarrow A [2 - 2 \cos \omega_0] = \sin \omega_0$$

$$\text{or } A = \frac{\sin \omega_0}{2 - 2 \cos \omega_0}; \quad B = \frac{\sin \omega_0}{2 \cos \omega_0 - 2}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

उ  
इ  
ए  
ओ  
क  
ख  
ग  
घ  
ङ  
च  
छ  
ज  
झ  
ञ  
ट  
ठ  
ड  
ढ  
ण  
त  
थ  
द  
ध  
न  
प  
फ  
ब  
भ  
म

$$\& c = \frac{1}{0.95} \left[ \frac{\sin \omega_0}{2 - 2 \cos \omega_0} \right]$$

$$\Rightarrow \frac{Y(z)}{z} = \frac{\sin \omega_0}{2 - 2 \cos \omega_0} \left[ \frac{1}{z - 0.95} + \frac{-z + 0.95}{z^2 - 2z \cos \omega_0 + 1} \right]$$

$$\frac{Y(z)}{z} = \frac{\sin \omega_0}{2(1 - \cos \omega_0)} \left[ \frac{1}{z - 0.95} + \frac{-(z - \cos \omega_0)}{(z - \cos \omega_0)^2 + (\sin \omega_0)^2} \right]$$

$$+ \frac{\sin \omega_0}{2(1 - \cos \omega_0)} \cdot \frac{0.95 - \cos \omega_0}{(z - \cos \omega_0)^2 + (\sin \omega_0)^2}$$

But we know that

$$ZT \{ \cos \omega_0 n u(n) \} = \frac{z(z - \cos \omega_0)}{z^2 - 2z \cos \omega_0 + 1}$$

$$\& ZT \{ \sin \omega_0 n u(n) \} = \frac{z \sin \omega_0}{z^2 - 2z \cos \omega_0 + 1}$$

$$\therefore \frac{Y(z)}{z} = \frac{\sin \omega_0}{2(1 - \cos \omega_0)} \left[ \frac{1}{z - 0.95} - \frac{z - \cos \omega_0}{z^2 - 2z \cos \omega_0 + 1} \right]$$

$$+ \frac{\sin \omega_0}{2(1 - \cos \omega_0)} \cdot \frac{(1 - \cos \omega_0)}{z^2 - 2z \cos \omega_0 + 1}$$

$$\Rightarrow y(n) = \frac{\sin \omega_0}{2(1 - \cos \omega_0)} \left[ (0.95)^n - \cos n \omega_0 \right] + \frac{1}{2} \cdot \sin \omega_0 n$$

$$y(n) = \frac{\sin \omega_0}{2(1 - \cos \omega_0)} (0.95)^n + \frac{1}{2} \left[ \sin \omega_0 n - \frac{\sin \omega_0 \cos \omega_0 n}{(1 - \cos \omega_0)} \right]$$


where  $\omega_0 = \pi/20$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
(Specimen Answer Booklet - For Practice Purpose Only)

उम्मीद  
इस हा  
नहीं रि  
चाहिए  
Cand  
must  
write  
marg

Q.7 (c)

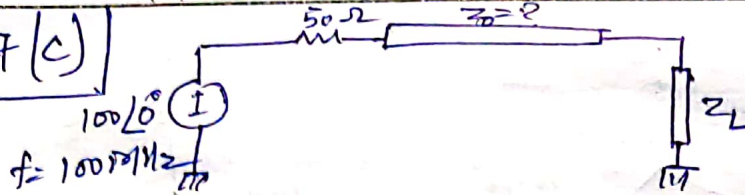

Now for the line;  $Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{0.25 \times 10^{-6}}{100 \times 10^{-12}}}$

$$Z_0 = 50 \Omega$$

$$\beta = \omega \sqrt{LC} = 2\pi \times 10^6 \times 100 \sqrt{2.5 \times 10^{-17}}$$

$$= 200\pi \times 10^4 \times 5 \times 10^{-9} \text{ m}^{-1}$$

$$\beta = \pi \text{ rad/m}$$

I) For  $Z_L = 50 \Omega$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = 0 \Rightarrow \Gamma = 0$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 1 \Rightarrow S = 1$$

$$Z_{in} = Z_0 \left[ \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \right] = \frac{Z_0 \times \cancel{[1 + j \tan \beta l]}}{\cancel{[1 + j \tan \beta l]}}$$

$$Z_{in} = 50 \Omega$$

II) For  $Z_L = 100 \Omega$

$$\Gamma = \frac{100 - 50}{100 + 50} = \frac{1}{3} \Rightarrow \Gamma = \frac{1}{3}$$

$$S = \frac{1 + \frac{1}{3}}{1 - \frac{1}{3}} = \frac{4/3}{2/3} \Rightarrow S = 2$$


$$Z_{in} = 50 \left[ \frac{100 + j50 \tan \pi \times 10^0}{50 + j100 \tan \pi \times 10^0} \right] = 100 \Omega$$

$$\text{or } Z_{in} = 100 \Omega$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

Q.3(a)

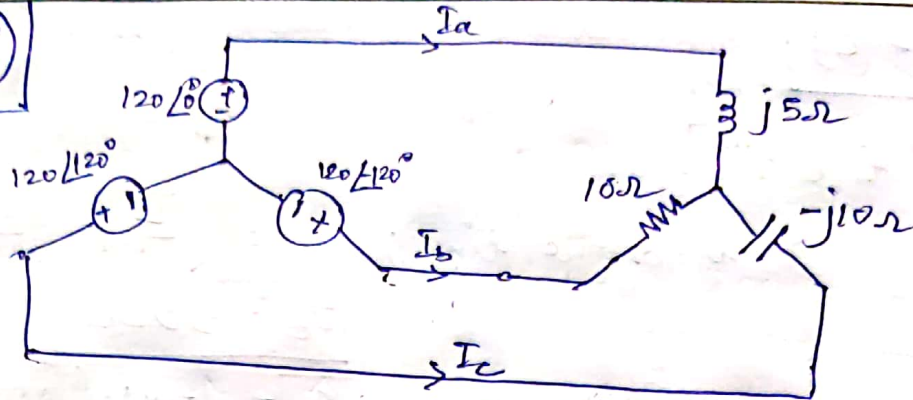

Now using KVL: -

$$120 - j5I_a + 10I_b - 120\angle 120^\circ = 0$$

$$\Rightarrow -jI_a + 10I_b = 207.85\angle -150^\circ \quad \text{--- (1)}$$

$$120 - j5I_a + (-j10)I_c - 120\angle 120^\circ = 0$$

$$\Rightarrow -j5I_a - j10I_c = 207.85\angle 150^\circ$$

Also  $120\angle -120^\circ - 10I_b + (-j10)I_c - 120\angle 120^\circ = 0$

$$\Rightarrow -10I_b - j10I_c = 207.85\angle 90^\circ$$

or 
$$\begin{bmatrix} -j & 10 & 0 \\ -j5 & 0 & -j10 \\ 0 & -10 & -j10 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 207.85\angle -150^\circ \\ 207.85\angle 150^\circ \\ 207.85\angle 90^\circ \end{bmatrix}$$

$$\Rightarrow (-j)^2 \begin{bmatrix} 1 & 10 & 0 \\ 5 & 0 & 10 \\ 0 & -10 & 10 \end{bmatrix} \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 207.85\angle -150^\circ \\ 207.85\angle 150^\circ \\ 207.85\angle 90^\circ \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} -0.25 & 0.25 & -0.25 \\ 0.125 & -0.25 & 0.025 \\ 0.125 & -0.025 & 0.125 \end{bmatrix} \begin{bmatrix} 1\angle -150^\circ \\ 1\angle 150^\circ \\ 1\angle 90^\circ \end{bmatrix} \times \frac{207.85}{-1}$$

# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\Rightarrow \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \frac{207.85}{-1} \begin{bmatrix} -0.25 \angle 150^\circ + 0.25 \angle 150^\circ - 0.25 \angle 90^\circ \\ 0.125 \angle -150^\circ - 0.25 \angle 150^\circ + 0.25 \angle 90^\circ \\ 0.125 \angle -150^\circ - 0.025 \angle 150^\circ + 0.125 \angle 90^\circ \end{bmatrix}$$
$$= \frac{207.85}{-1} \begin{bmatrix} 0 \\ 0.125 \angle 30^\circ \\ 0.1 \angle 150^\circ \end{bmatrix}$$

$$\Rightarrow \boxed{I_a = 0 ; I_b = -25.98 \angle 30^\circ ; I_c = -20.79 \angle 150^\circ}$$

For total complex power :-

$$S = V_A I_A^* + V_B I_B^* + V_C I_C^*$$

$$= 120 \times 0 + 120 \angle -120^\circ \cdot (-25.98 \angle -30^\circ)$$

$$+ (120 \angle 120^\circ \cdot (-20.79 \angle -150^\circ))$$

$$= 3117.6 \angle 30^\circ + 2494.8 \angle 150^\circ \text{ VA}$$

$$\boxed{S = 2857.56 \angle 79.12^\circ \text{ VA}}$$



# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)

$$\text{Q3(b)} / (i) \eta = 200 \angle 30^\circ$$

$$\text{Now } \vec{H} = 10 e^{-\alpha x} \cdot \cos(\omega t - \frac{1}{2}x) \hat{a}_y \text{ A/m}$$

$$\text{We know } \frac{E_0}{H_0} = |\eta| \Rightarrow \boxed{E_0 = 2000 \text{ V/m}}$$

$$\& \hat{a}_E = -\hat{a}_x \times \hat{a}_H = -\hat{a}_x \times \hat{a}_y = -\hat{a}_z$$

$$\Rightarrow \vec{E} = -2000 e^{-\alpha x} \cos(\omega t - \frac{1}{2}x) \hat{a}_z \text{ V/m}$$

$$\text{Now } \beta = 0.5 \text{ \& we know } \frac{\sigma}{\omega \epsilon} = \tan \theta$$
$$= \tan(2 \times 30^\circ)$$
$$= \sqrt{3}$$

$$\text{So, } \gamma = \sqrt{j\omega\mu(\sigma + j\omega\epsilon)} = \sqrt{j\omega\mu j\omega\epsilon (1 - j\frac{\sigma}{\omega\epsilon})}$$

$$= j\omega \sqrt{\mu\epsilon} \cdot \sqrt{1 - j\sqrt{3}}$$

$$= j\omega \sqrt{\mu\epsilon} \cdot \sqrt{2} \angle -30^\circ$$

$$\gamma = \frac{1}{2} \times \sqrt{2} \times \angle -30 + 90^\circ = \frac{1}{\sqrt{2}} \angle 60^\circ$$

$$\Rightarrow \alpha = \frac{1}{\sqrt{2}} \cos 60; \quad \beta = \frac{1}{\sqrt{2}} \sin 60$$

$$\text{or } \boxed{\alpha = 0.354 \text{ m}^{-1}}$$


$$\text{skin depth} = \frac{1}{\alpha} = \boxed{2.825 \text{ m}}$$

direction of wave polarization =  $\hat{a}_z$

$$\boxed{\vec{E} = -2000 e^{-0.354x} \cos(\omega t - \frac{x}{2}) \hat{a}_z \text{ V/m}}$$
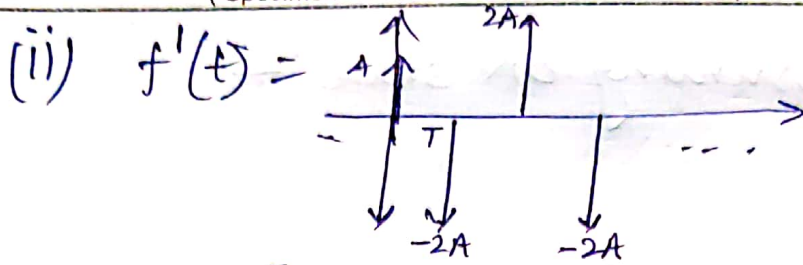
# UPSC

Answer Questions in NOT MORE THAN the Word Limit specified for each in the Parenthesis.  
Content of the Question is more important than length.  
( Specimen Answer Booklet - For Practice Purpose Only)



$$\begin{aligned} \text{or } f'(t) &= A[\delta(t) - 2\delta(t-T) + 2\delta(t-2T) - 2\delta(t-3T) \dots] \\ &= A\delta(t) - 2A[\delta(t-T) + \delta(t-3T) + \delta(t-5T) + \dots] \\ &\quad + 2A[\delta(t-2T) + \delta(t-4T) + \dots] \end{aligned}$$

Now taking Laplace transform:—

$$\begin{aligned} s.F(s) &= A - 2A[e^{-sT} + e^{-3sT} + e^{-5sT} + \dots] \\ &\quad + 2A[e^{-2sT} + e^{-4sT} + \dots] \\ &= A - 2A \cdot \frac{e^{-sT}}{1 - e^{-2sT}} + 2A \frac{e^{-2sT}}{1 - e^{-2sT}} \\ &= \frac{1 - e^{-2sT} - 2e^{-sT} + 2e^{-2sT}}{1 - e^{-2sT}} = \frac{1 - 2e^{-sT} + e^{-2sT}}{1 - e^{-2sT}} \\ &= \frac{(1 - e^{-sT})^2}{(1 - e^{-sT})(1 + e^{-sT})} = \frac{1 - e^{-sT}}{1 + e^{-sT}} \end{aligned}$$

$$\text{or } F(s) = \frac{1}{s} \cdot \frac{1 - e^{-sT}}{1 + e^{-sT}}$$