

CMOS Power Consumption



Lecture 13

18-322 Fall 2003

Textbook: [Sections 5.5 5.6 6.2 (p. 257-263) 11.7.1]

Overview



- Low-power design

- ☒ Motivation

- ☒ Sources of power dissipation in CMOS

- ☒ Power modeling


- ☒ Optimization Techniques (a survey)

Why worry about power?

-- Heat Dissipation



Power Density Trends

 

Surpassed hot-plate power density in 0.5µ

Not too long to reach nuclear reactor


High End Power Consumption



- While you can probably afford to pay for 100-200W of power for your desktop...
- Getting that heat off the chip and out of the box is expensive

A Booming Market: Portable Devices


What we would need...

 

■ What we'd like...


- ☒ Video decompression
- ☒ Speech recognition
- ☒ Protocols, ECC, ...
- ☒ Handwriting recognition
- ☒ Text/Graphics processing
- ☒ Java interpreter

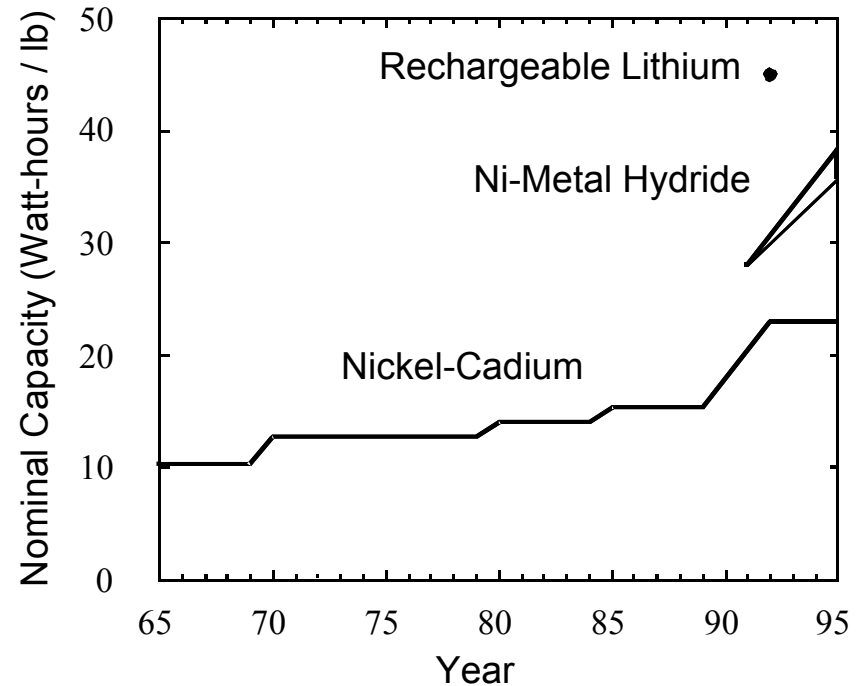■ **Up to 1 month of uninterrupted operation!**



Expected Battery Lifetime increase over next 5 years: 30-40%

Where Does Power Go in CMOS?

 

- **Switching power:** due to charging and discharging of output capacitances:

$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$


- Short-circuit power: due to non-zero rise/fall times
- Leakage power (important with decreasing device sizes)
 - ⊗ Typically between 0.1nA - 0.5nA at room temperature

Short-Circuit Power


- Inputs have finite rise and fall times

☒ Depends on device sizes

 - Direct current path from V_{DD} to GND while PMOS and NMOS are ON simultaneously for a short period



Leakage Current

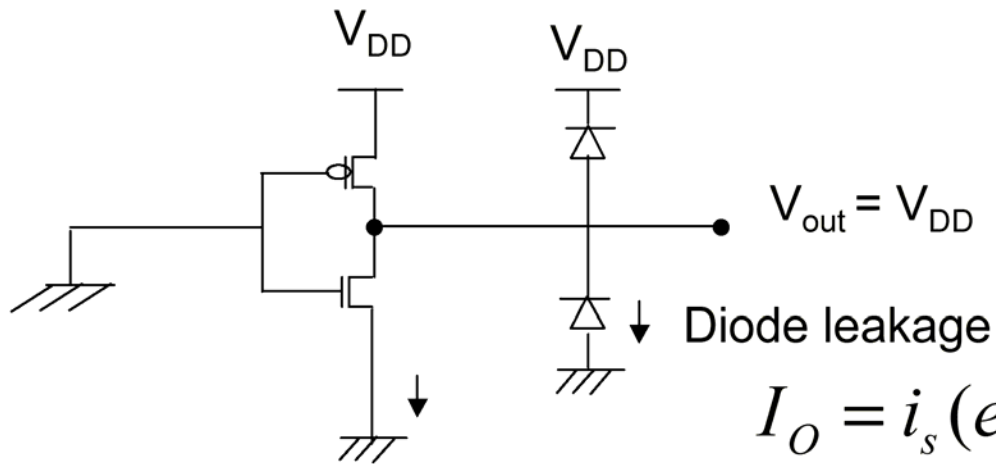


$$I_O = i_s (e^{Vq/kT} - 1)$$

Sub-threshold current

$$I_D = K \cdot e^{(V_{gs} - V_t)q/nkT} (1 - e^{V_{ds}q/kT})$$

New Problem: Gate Leakage

 - Now about 20-30% of all leakage, and growing
- Gate oxide is so thin, electrons tunnel thru it...
- NMOS is much worse than PMOS



Gate/Circuit-Level Power Estimation

■ It is a very difficult problem

☒ Challenges

☒ V_{DD} , f_{clk} , C_L are known

- Actually, the layout will determine the interconnect capacitances

☒ Need *node-by-node* accuracy

- Power dissipation is highly data-dependent

☒ Need to estimate switching activity accurately

- Simulation may take days to complete

Dynamic Power Consumption - Revisited

Power = Energy/transition * transition rate

$$= C_L * V_{dd}^2 * f_{0 \rightarrow 1}$$

$$= C_L * V_{dd}^2 * P_{0 \rightarrow 1} * f$$

$$= C_{EFF} * V_{dd}^2 * f$$

$$P = C_L (V_{dd}^2 / 2) f_{clk} SW$$

Switching activity (factor)
on a signal line

$$C_{EFF} = \text{Effective Capacitance} = C_L * P_{0 \rightarrow 1}$$

Power Dissipation is Data Dependent
Function of *Switching Activity*

Example: Static 2 Input NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of 2 input NOR gate

Assume:

$$P(A=1) = 1/2$$


$$P(B=1) = 1/2$$

Then:

$$P(\text{Out}=1) = 1/4 \text{ (this is the *signal probability*)}$$

$$P(0 \rightarrow 1) = P(\text{Out} = 0) \cdot P(\text{Out} = 1) \\ = 3/4 \times 1/4 = 3/16 \text{ (this is the *transition probability*)}$$


$$C_{\text{EFF}} = 3/16 C_L$$

 

$$P(\text{Out}=1) = ?$$

$$P(0 \rightarrow 1) = ?$$

Power Consumption *is* Data Dependent

 

0→0	0→0	1→1
0→0	0→1	1→0
0→0	1→0	0→1
0→0	1→1	0→0
0→1	0→0	1→0
0→1	0→1	1→0
0→1	1→0	0→0
0→1	1→1	0→0
1→0	0→0	0→1
1→0	0→1	0→0
1→0	1→0	0→1
1→0	1→1	0→0
1→1	0→0	0→0
1→1	0→1	0→0
1→1	1→0	0→0
1→1	1→1	0→0

Suppose now that only patterns 00 and 11 can be applied (w/ equal probabilities). Then:

0→0	0→0	1→1
0→1	0→1	1→0
1→0	1→0	0→1
1→1	1→1	0→0

$\Rightarrow P(0 \rightarrow 1) = 1/4$

Similarly, suppose that every 0 applied to the input A is immediately followed by a 1 while every 1 applied to B is immediately followed by a 0. $P(0 \rightarrow 1) = ?$


Transition Probabilities for Basic Gates

	$P_{0 \rightarrow 1}$
AND	$(1 - P_A P_B) P_A P_B$
OR	$(1 - P_A)(1 - P_B)(1 - (1 - P_A)(1 - P_B))$
EXOR	$(1 - (P_A + P_B - 2P_A P_B))(P_A + P_B - 2P_A P_B)$

Switching Activity for Static CMOS

$$P_{0 \rightarrow 1} = P_0 \cdot P_1$$

(Big) Problem: Re-convergent Fanout

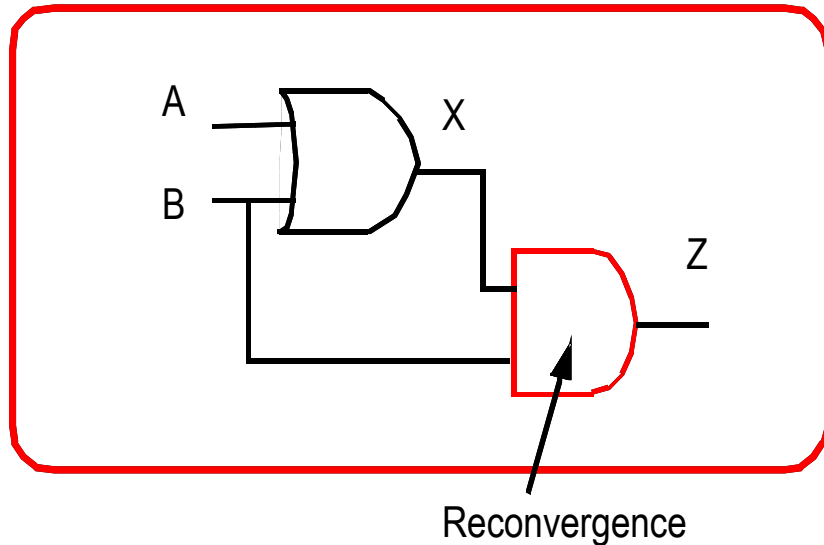



In this case, $Z = B$ as it can be easily seen. The previous analysis simply fails because the signals are not independent!

$$P(Z=1) = P(B=1) \cdot P(X=1 \mid B=1) = P(B=1)$$



Main issue: Becomes complex and intractable real fast!

Another (Big) Problem: Glitching in Static CMOS


also called: dynamic hazards

  

Example: A Chain of NAND Gates

  


Glitch Reduction Using Balanced Paths

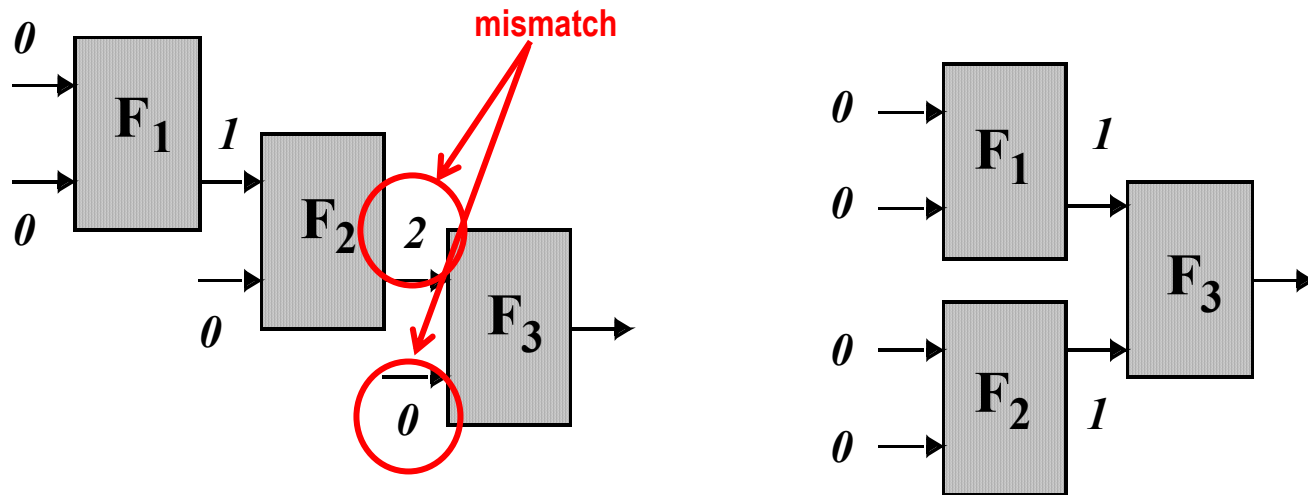

Equalize Lengths of Timing Paths Through Design

Delay is important: Delay vs. V_{DD} and V_T

 Think about (Power \times Delay) product!




- Delay for a 0- \rightarrow 1 transition to propagate to the output:

$$t_{pLH} = \frac{C_L V_{DD}}{k_n (V_{DD} - V_{Tn})^2}$$

- ☒ Similar for a 1- \rightarrow 0 transition

Delay vs. V_{DD}

 

Power-Performance Trade-offs

■ Prime choice: V_{DD} reduction

- ☒ In recent years we have witnessed an increasing interest in supply voltage reduction (e.g. Dynamic Voltage Scaling)
 - High V_{DD} on critical path or for high performance
 - Low V_{DD} where there is some available slack
- ☒ Design at very low voltages is still an open problem (0.6 – 0.9V by 2010!)
 - Ensures lower power
 - ... but higher latency – loss in performance

■ Reduce switching activity

- ☒ Logic synthesis
- ☒ Clock gating

■ Reduce physical capacitance


- ☒ Proper device sizing
- ☒ Good layout

How about POWER?



Ways to reducing power consumption

- Load capacitance (C_L)
 - ☒ Roughly proportional to the chip area
- Switching activity (avg. number of transitions/cycle)
 - ☒ Very data dependent
 - ☒ A big portion due to glitches (real-delay)
- Clock frequency (f)
 - ☒ Lowering only f decreases average power, but total energy is the same and throughput is worse

 - Voltage supply (V_{DD})
 - Biggest impact



Using parallelism (1)

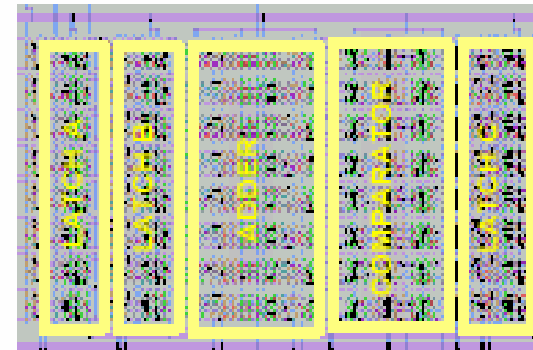
 


Area = $636 \times 833 \mu^2$

$$P_{\text{ref}} = C_{\text{ref}} V_{\text{DD}}^2 f_{\text{ref}}$$

Assume: $t_p = 25\text{ns}$ (worst-case, *all* modules) at $V_{\text{DD}} = 5\text{V}$

Using parallelism (2)

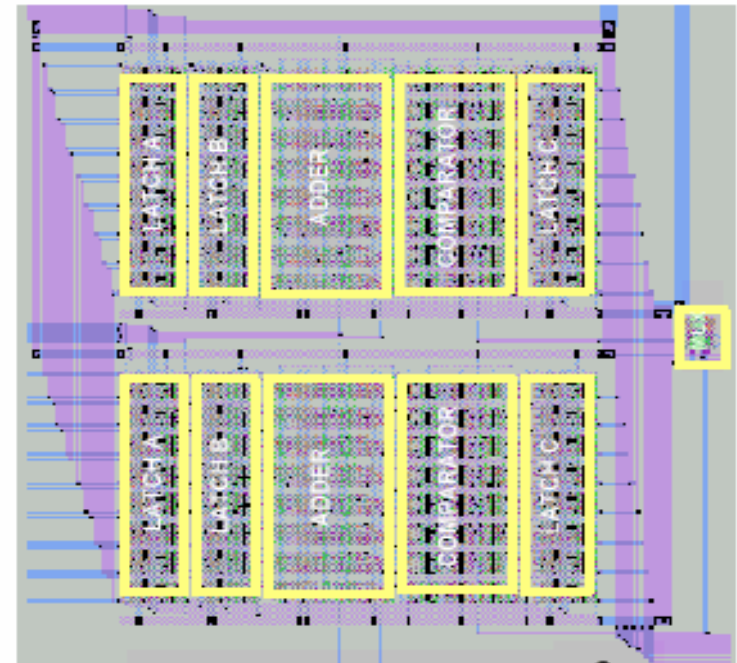
 


Area = 1476 x 1219 μ^2

Area increases about 3.4 times!

- $C_{\text{par}} = 2.15C$ (extra-routing needed)
- $f_{\text{par}} = f/2$ ($t_{p,\text{new}} = (50)\text{ns} \Rightarrow V_{\text{DD}} \sim 2.9\text{V}$; $V_{\text{DD,par}} = 0.58 V_{\text{DD}}$)
- $P_{\text{par}} = C_{\text{par}} V_{\text{DD}}^2 f_{\text{par}} = 0.36 P_{\text{ref}}$


Using pipelining

  

Area = $640 \times 1081 \mu^2$

- $C_{\text{pipe}} = 1.15C$
- Delay decreases 2 times ($V_{DD,\text{pipe}} = 0.58 V_{DD}$)
- $P_{\text{pipe}} = 0.39 P$

Chain vs. balanced design

 

■ Question for you:


☒ Which of the two designs is more energy efficient?

☒ Assume:

- Zero-delay model
- All inputs have a signal probability of 0.5

☒ Hint: Calculate $p_{0 \rightarrow 1}$ for W, X and F

Chain vs. balanced design

 

■ For the zero-delay model

☒ Chain design is better




☒ But ignores **glitching**

☒ Depending on the gate delays, the chain design may be worse

Low energy gates – transistor sizing



- Use the *smallest transistors* that satisfy the delay constraints
 - ☒ Increasing transistor size improves the speed but it also increases power dissipation (since the load capacitances increases)
 - ☒ Slack time - difference between required time and arrival time of a signal at a gate output
 - Positive slack - size down
 - Negative slack - size up
- Make gates that toggle more frequently smaller

Low energy gate netlists – pin ordering

   

- Better to postpone the introduction of signals with a high transition rate (signals with signal probability close to 0.5)


Control circuits

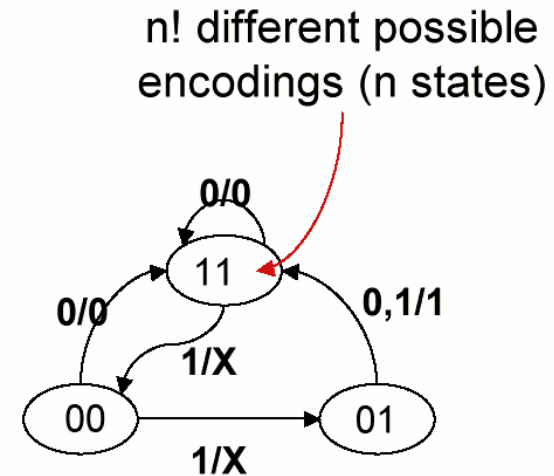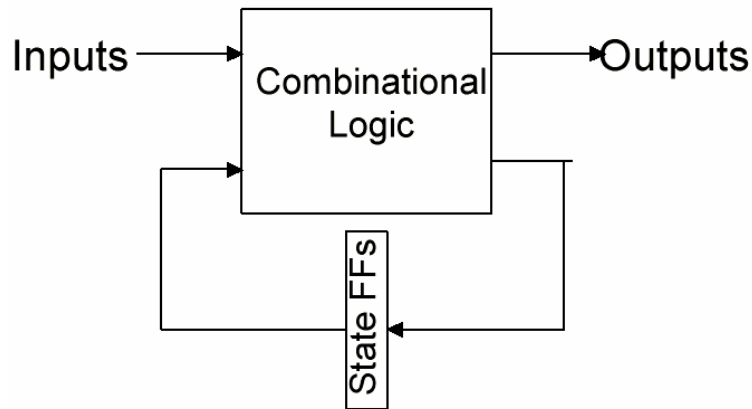


- State encoding has a **big impact** on the power efficiency
- **Energy driven** -> try to minimize number of bit transitions in the state register
 - ☒ Fewer transitions in state register
 - ☒ Fewer transitions propagated to combinational logic

Bus encoding

- Reduces number of bit toggles on the bus
- Different flavors
 - ☒ Bus-invert coding
 - ☒ Uses an extra bus line *invert*:
 - if the number of transitions is $< K/2$, invert = 0 and the symbol is transmitted as is
 - if the number of transitions is $> K/2$, invert = 1 and the symbol is transmitted in a complemented form
 - ☒ Low-weight coding
 - ☒ Uses *transition* signaling instead of *level* signaling

 

Bus invert coding

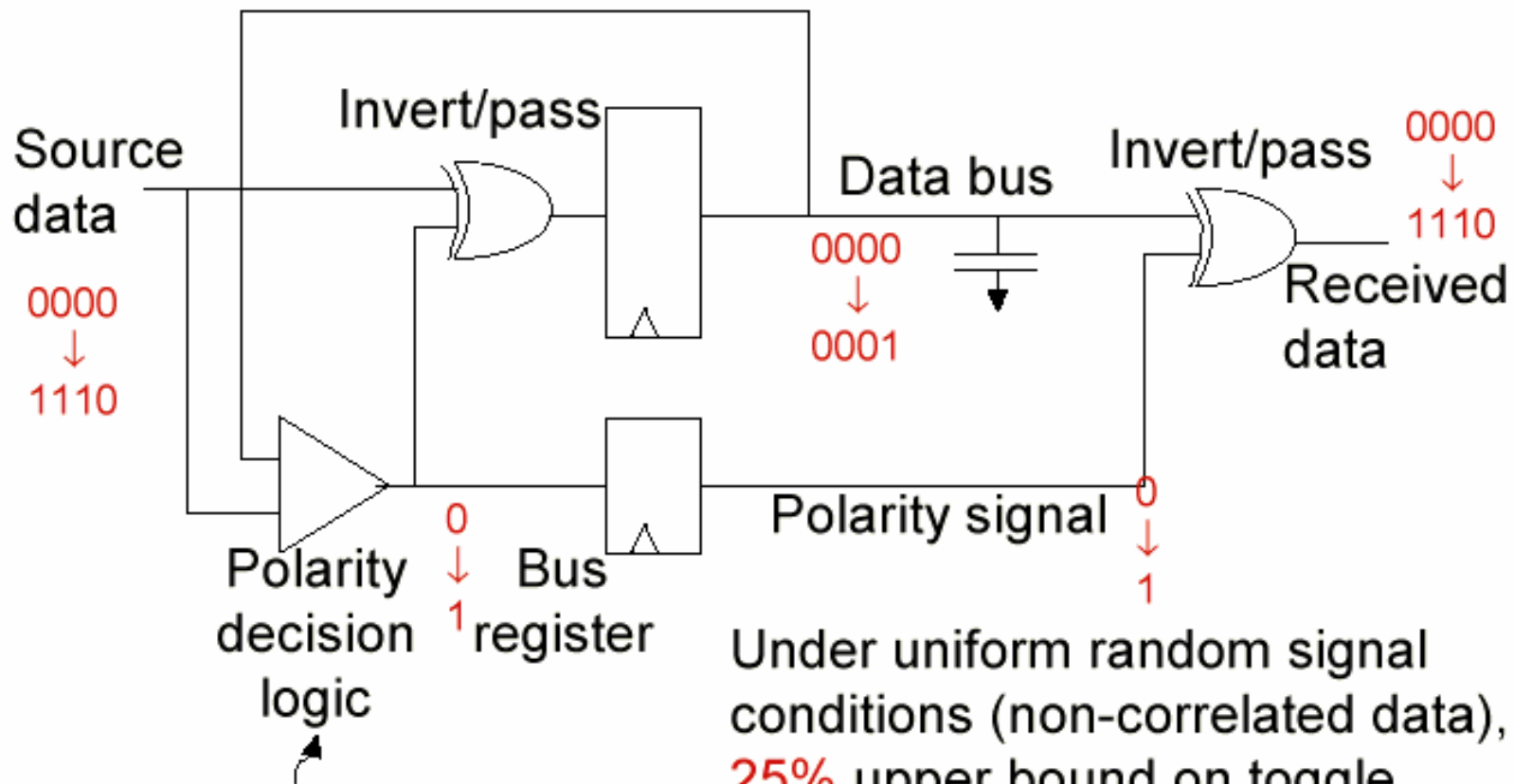


Hamming distance

Under uniform random signal conditions (non-correlated data), **25%** upper bound on toggle reduction

Summary

 - Power Dissipation is already a **prime design constraint**
- Low-power design requires operation at lowest possible voltage and clock speed
- Low-power design requires optimization at all levels of abstraction



Announcements



- Project M1:

- ☑ Check off in lab session

- ☑ Report by Friday

- Exam Review Session:

- ☑ Monday Oct 13, 4:30-6:30pm

- ☑ PH 125C